




COMBINATIONAL CIRCUITS

Combinational logic

- A **combinational circuit** consists of logic gates whose outputs at any time are determined directly from the present combination of inputs without regard to previous outputs.
- A **combinational circuit** performs a specific information processing operation fully specified logically by a set of Boolean functions.
- A **Combinational circuit** consists of input variables, logic gates, and output variables.

Combinational logic

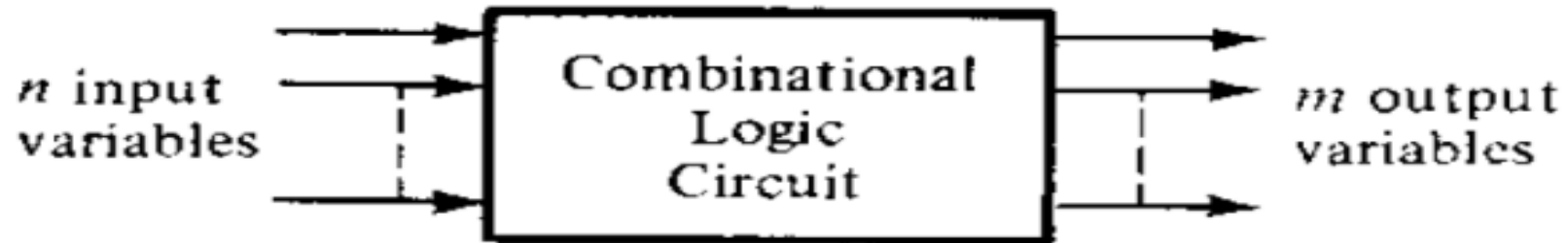- The logic gate accept signals from the inputs and generate signals to the outputs.
- This process transforms binary information from the given input data to the required output data.



Combinational logic

■ Design Procedures

- Starts from the verbal outline of the problem and ends in a logic circuit diagram.
- The procedure involves the following step,
 - The problem is stated.
 - Input and required output variables are determined.
 - Assigned the variables letter symbols.
 - Make the truth table.
 - The simplified Boolean functions for each output is obtained.
 - The logic diagram is drawn.

Combinational logic

■ Adders

- Adders are important in computers and also in other types of digital systems in which numerical data are processed.
- An understanding of the basic adder operation is fundamental to the study of digital systems.
- The most basic operation is no doubt is the addition of two binary digits.

The Half Adder

■ Half Adder

- The combinational circuit that performs the additions of two bit is called Half adder.
- One that performs the addition of three bits including two digits and one previous carry is a full adder.
- Two half adders can be employed to form a full adder.

Combinational logic

■ Half Adder


- It has two inputs and two outputs.
- The input variables designate the augends and addend bits; the output variables produce the sum and carry.
- It is necessary to specify two output variables because the result may consist of two binary digits.
- A and B are two input binary variables while C and S used for carry and Sum to the outputs.

Combinational logic

■ Half Adder

- The half-adder accepts two binary digits on its inputs and produces two binary digits on its outputs, a sum bit and a carry bit.
- The truth table look like this,

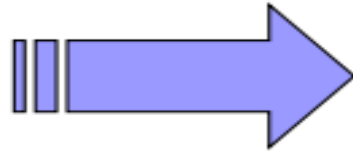$0 + 0 = 0$
$0 + 1 = 1$
$1 + 0 = 1$
$1 + 1 = 10$




A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Combinational logic

■ Half Adder

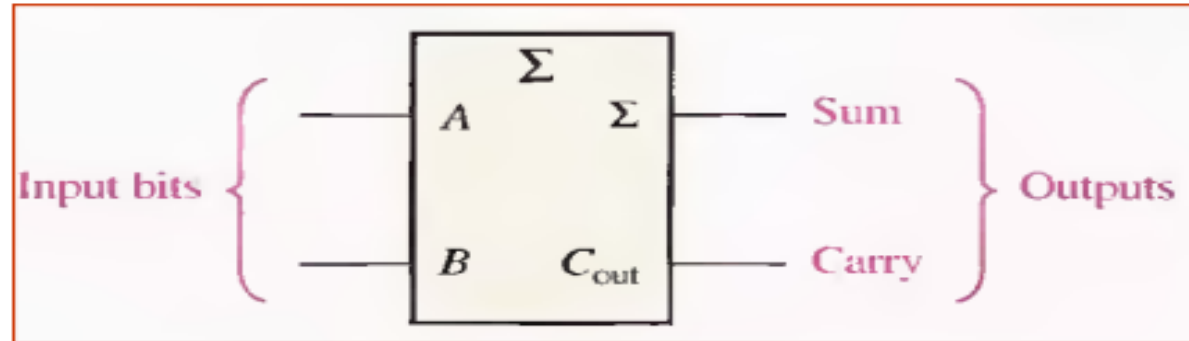- A half-adder is represented by the logic symbol in Figure below,



Half Adder

■ Half-Adder Logic

- Notice that the output Carry (C_{out}) is a 1 only when both A and B are 1s; therefore C_{out} can be expressed as the AND of the input variables.
- $C_{out} = AB$
- Now observe that the sum output (Σ) is a 1 only if the input variables, A and B, are not equal.
- The sum can therefore be expressed as the exclusive-OR of the input variables.

$$\Sigma = A \oplus B$$


Related Example

■ Half-Adder Logic




- The logic implementation required for the half adder function can be developed.
- The output carry is produced with an AND gate with A and B on the inputs.
- The sum output is generated with an exclusive-OR gate.

Half Adder

- Half-Adder Logic diagram

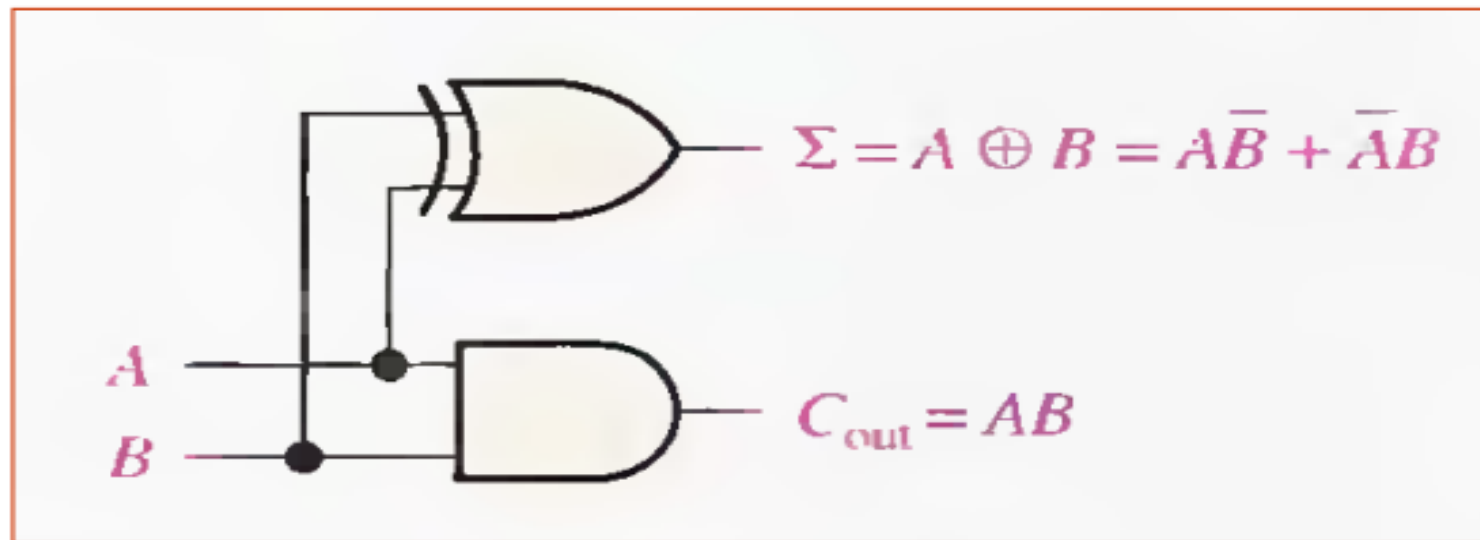

Solutions

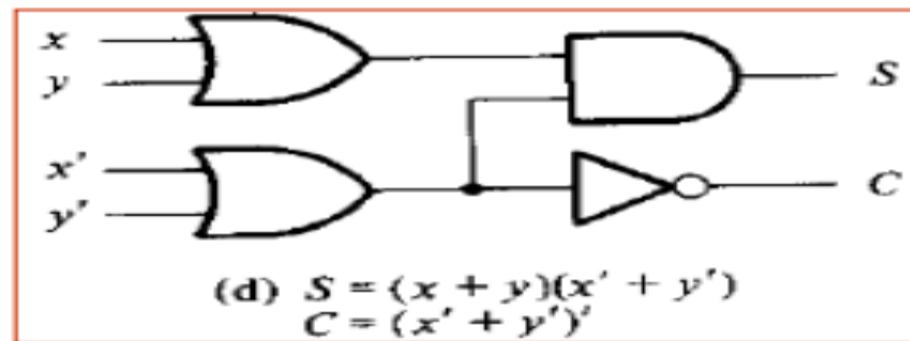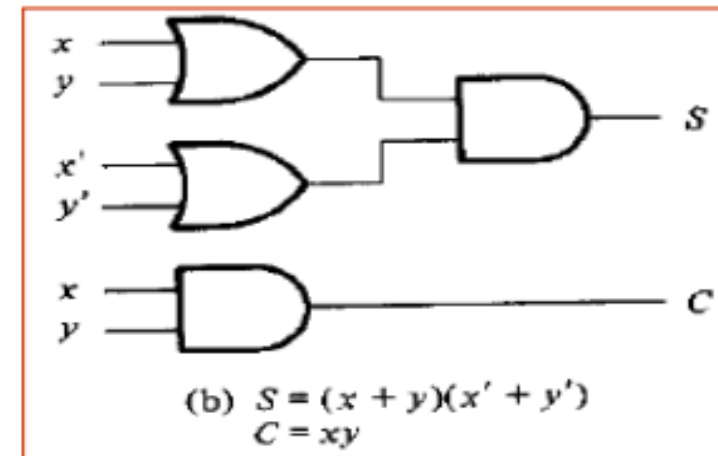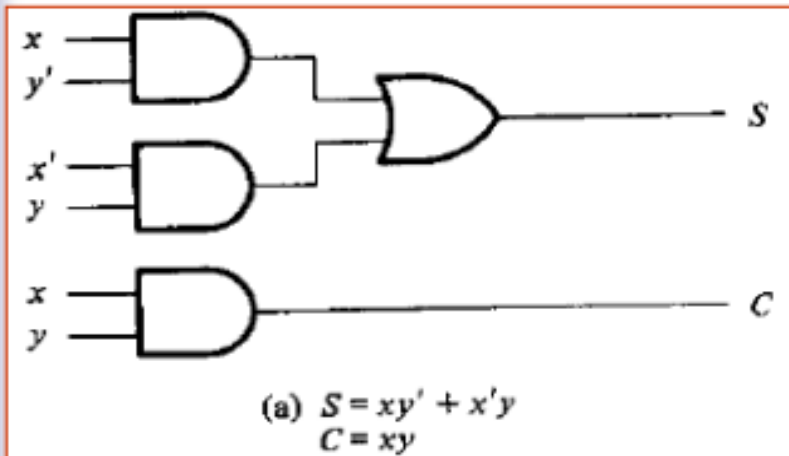


Full Adder

■ Full Adder

- The second category of adder is the full-adder.
- The full-adder accepts two input bits and an input carry and generates a sum output and an output carry.
- The basic difference between a full-adder and a half-adder is that the full-adder accepts an input carry.

Full Adder

- Logical symbol for full adder is,

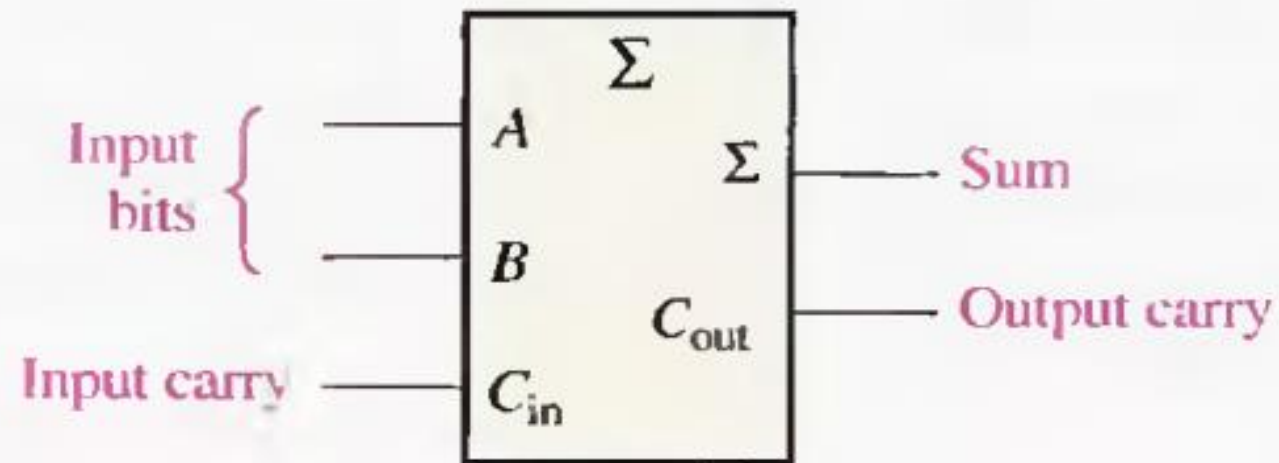

Full Adder

Truth Table

A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C_{in} = input carry, sometime designated as CI

C_{out} = output carry sometimes designated as CO

Σ =sum

A and B = input variables (operands)

Full Adder

■ Full Adder Logic

- The full-adder must add the two input bits and the input carry.
- From the half-adder you know that the sum of the input bits A and B is the exclusive-OR of those two variables, A xor B.
- For the input carry (C_{in}) to be added to the input bits. it must be exclusive-ORed with A xor B, yielding the equation for the sum output of the full-adder.

$$\Sigma = (A \oplus B) \oplus C_{in}$$

Full Adder

- Map for Full Adder (For Sum Function)

		yz			
		00	01	11	10
x	0		1		1
	1	1		1	

$$S = x'y'z + x'yz' + xy'z' + xyz$$


Full Adder

For Carry Simplified Expression

		yz			
x		00	01	11	10
	0			1	
	1		1	1	1

$$C = xy + xz + yz$$


Implementation of Full Adder in SOP

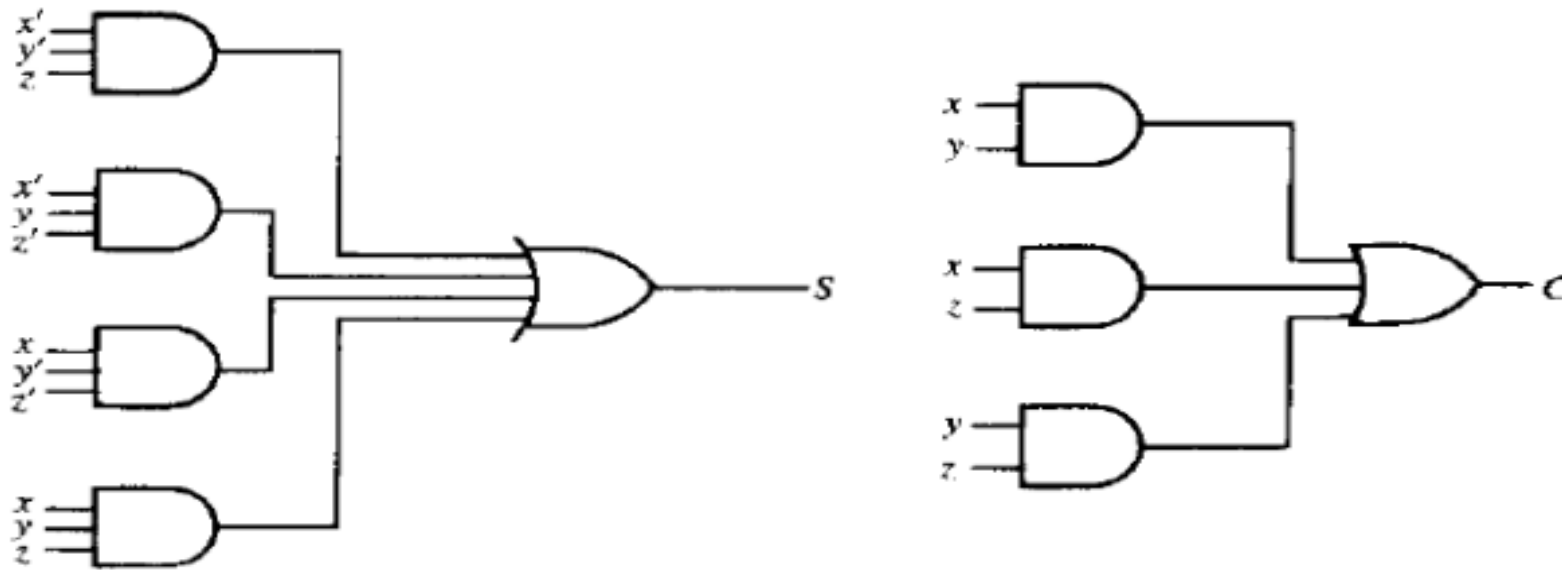

Logic Diagram

Implementation of Full Adder

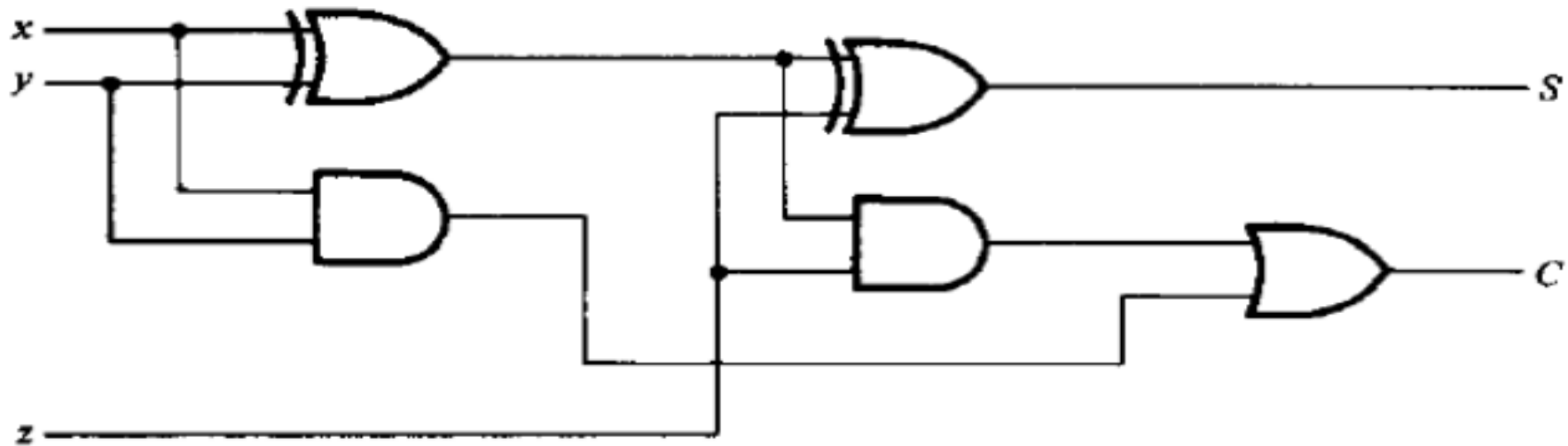Implementation of a full adder with two half adders and an OR Gate



Adders

$$S = z \oplus (x \oplus y)$$

$$= z'(xy' + x'y) + z(xy' + x'y)'$$


$$= z'(xy' + x'y) + z(xy + x'y')$$

$$= xy'z' + x'yz' + xyz + x'y'z$$

$$C = z(xy' + x'y) + xy = xy'z + x'yz + xy$$

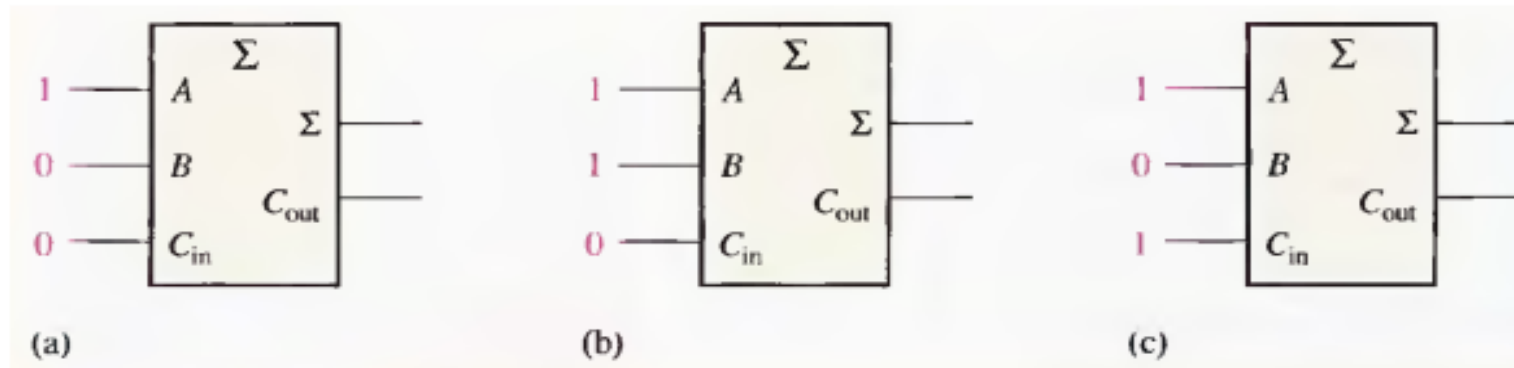Problem

- For each of the three full-adders in Figure below, determine the outputs for the inputs shown.



Solution

(a) The input bits are $A = 1$, $B = 0$, and $C_{in} = 0$.

$$1 + 0 + 0 = 1 \text{ with no carry}$$

Therefore, $\Sigma = 1$ and $C_{out} = 0$.

(b) The input bits are $A = 1$, $B = 1$, and $C_{in} = 0$.

$$1 + 1 + 0 = 0 \text{ with a carry of } 1$$

Therefore, $\Sigma = 0$ and $C_{out} = 1$.

(c) The input bits are $A = 1$, $B = 0$, and $C_{in} = 1$.

$$1 + 0 + 1 = 0 \text{ with a carry of } 1$$

Therefore, $\Sigma = 0$ and $C_{out} = 1$.



THANK YOU