

xDate: Feb 11, 2026

Lab # 02 TO UNDERSTAND THE CONCEPT OF UNIVERSAL NAND AND NOR GATES IN DIGITAL CIRCUIT DESIGN

OBJECTIVES:

O1: To understand the concept of universal NAND and NOR Gates

O2: To implement Logic Circuits using only NAND or NOR gates.

BACKGROUND THEORY

Because the NAND function has functional completeness all logic systems can be converted into NAND gates. This is also true for NOR gates. In principle, any combinatorial logic function can be realized with enough NAND gates and/or NOR Gates.

NAND GATE EQUIVALENT OF BASIC LOGIC GATE

NOT Gate:

A NOT gate is made by joining the inputs of a NAND gate together. Since a NAND gate is equivalent to an AND gate followed by a NOT gate, joining the inputs of a NAND gate leaves only the NOT gate.

Desired NOT Gate NAND Construction



AND Gate:

An AND gate is made by following a NAND gate with a NOT gate as shown below.


Desired AND Gate NAND Construction



OR Gate:

If the truth table for a NAND gate is examined or by applying De Morgan's Laws, it can be seen that if any of the inputs are 0, then the output will be 1. To be an OR gate, however, the output must be 1 if any input is 1. Therefore, if the inputs are inverted, any high input will trigger a high output.


Desired OR Gate NAND Construction

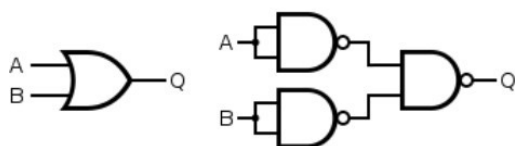

NOR Gate:

A NOR gate is simply an inverted OR gate. Output is high when neither input A nor input B is high:


Desired NOR Gate NAND Construction

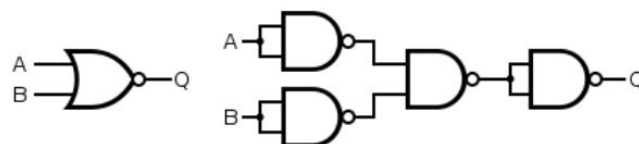

XOR Gate:

An XOR gate is constructed similarly to an OR gate, except with an additional NAND gate inserted such that if both inputs are high, the inputs to the final NAND gate will also be high, and the output will be low.


Desired XOR Gate NAND Construction

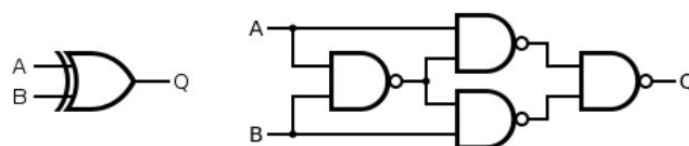

XNOR Gate:

An XNOR gate is simply an XOR gate with an inverted output:

Desired XNOR Gate NAND Construction

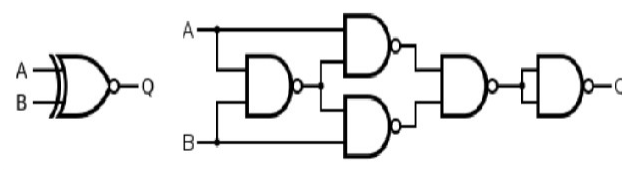

NOR GATE EQUIVALENT OF BASIC LOGIC GATES

NOT Gate:

Same as that in NAND Logic, shorting the inputs of a NOR gate gets us a NOT gate:

Desired Gate


NOR Construction

OR Gate:

The OR gate is simply a NOR gate followed by another NOR gate.

Desired Gate


NOR Construction

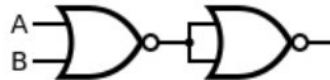

AND Gate:

Desired Gate



NOR Construction

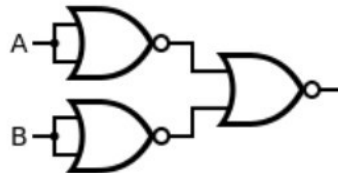

A NAND gate is made using an AND gate in series with a NOT gate:

Desired Gate


NOR Construction

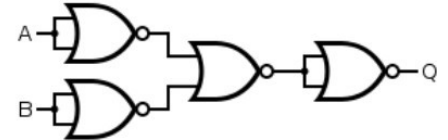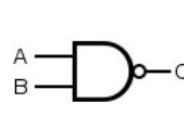

XOR Gate:

Desired Gate


NOR Construction

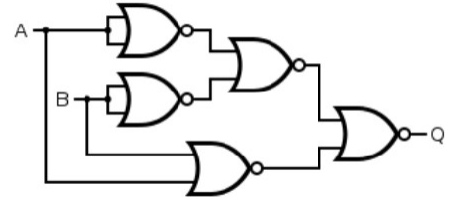

XNOR Gate:

Desired XNOR Gate

NOR Construction

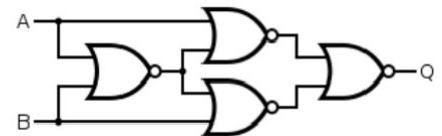

NAND Gate:

AND OR INVERTER (AOI) TO NAND GATE CONVERSION STEPS

- 1) If starting from a logic expression, implement the design with AOI logic.
- 2) In the AOI implementation, identify and replace every AND, OR, and INVERTER gate with its NAND equivalent.
- 3) Redraw the circuit.
- 4) Identify and eliminate any double inversions (i.e., back-to-back inverters).
- 5) Redraw the final circuit.
- 6) Example conversion:

Boolean expression to be converted into Universal NAND equivalent:

$$f(c) = A + \bar{B} + C$$

1. Implement the circuit using AOI Logic:

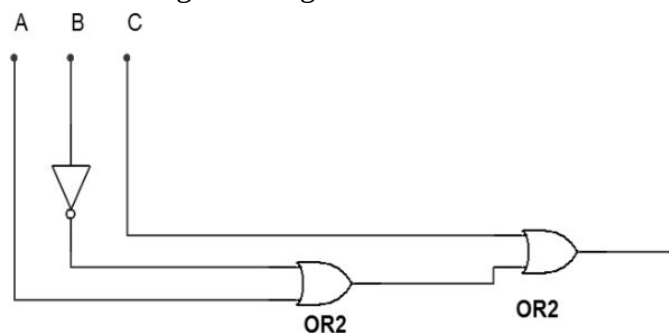


Fig 2.1: AOI Implementation of Boolean expression

2. Identify and replace every AND, OR and/or NOT gate with its NAND equivalent.

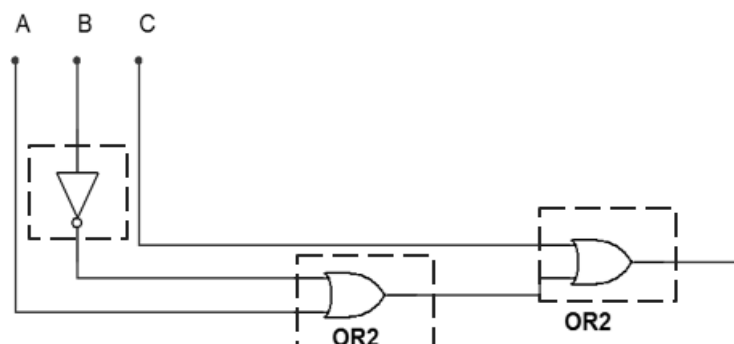


Fig 2.2: Identifying gates to be replaced

3. Redraw the circuit (using NAND counterparts).

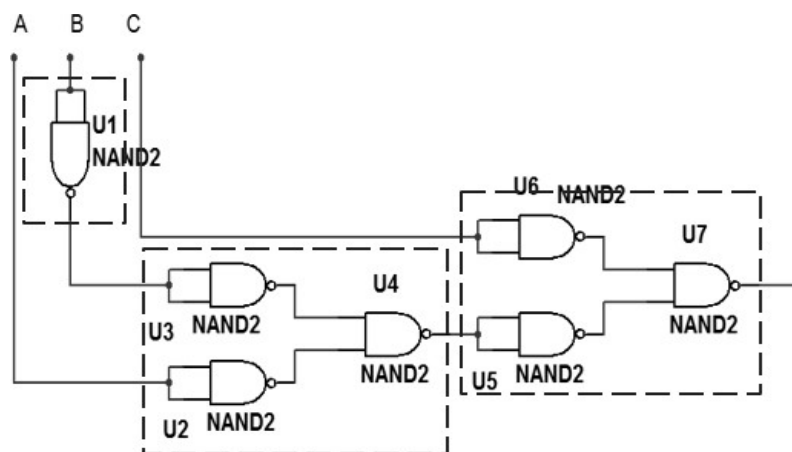


Fig 2.3: AOI replaced with NAND gates

4. Identify and eliminate any double inversions (i.e. back-to-back inverters).

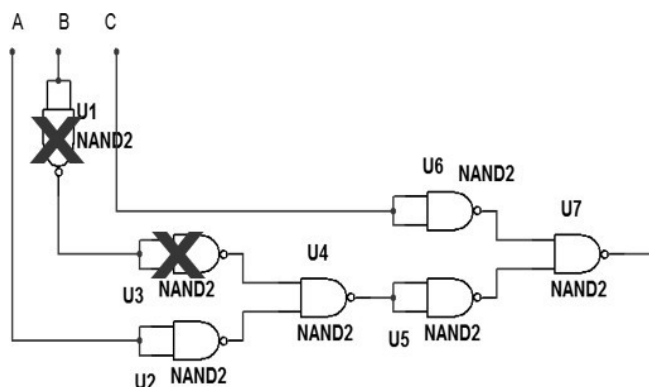


Fig 2.4: Eliminating double Inversions

5. Redraw the final circuit.

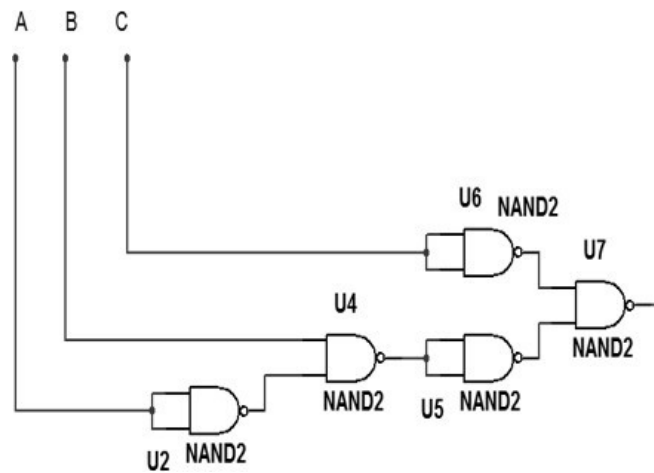


Fig 2.4: Final Circuit

6. The same procedure can be followed for conversion of AOI gates to Universal NOR Gates

LAB TASK

Consider the Boolean expression given below:

$$X = A(B + \bar{C})$$

- Construct an AOI circuit for the expression and develop its Truth Table
- Convert the circuit into its Universal NAND equivalent
(Attach working on separate sheet). NAND Gate equivalent of the given expression:

Input A	Input B	Input C	Output Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Table 2.1: Truth table for the AOI circuit

Input A	Input B	Input C	Output Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Table 2.2: Truth table for NAND equivalent based Hardware circuit**HARDWARE REQUIRED:**

- Power supply with cables
- Breadboard
- Logic gate ICs: 1) NAND Gate
- LEDs
- Logic Probe (optional)

PROCEDURE:

1. Construct the NAND equivalent circuit on bread board.
2. Apply inputs and check corresponding Outputs.
3. Note the readings in Table 2.2
4. compare the two tables 2.1 and 2.2
5. Was the conversion successful? If yes, Design the equivalent circuit for the following expression using Universal NOR Gate (attach working on separate sheet):

$$X = \overline{A}B + \overline{C}D$$

NOR Gate equivalent of the given expression:

Input A	Input B	Input C	Output Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Table 2.3: Truth table for the AOI circuit

Input A	Input B	Input C	Output Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Table 2.4: Truth table for NOR equivalent circuit.**CONCLUSION (What have you learnt from this experiment?):**

Universal Gate Concept: I learned that NAND and NOR gates are called "universal gates" because they have functional completeness. This means any Boolean function or logic circuit can be implemented using only NAND gates or only NOR gates. We don't need AND, OR, or NOT gates if we have NAND or NOR gates available.

LEARNING OUTCOMES

Upon successful completion of the lab, students will be able to:

LO1: Understand the importance of NAND and NOR Gates as Universal gates.

LO2: Apply the rules of converting AOI Gates to their Universal NAND or Universal NOR equivalents.

